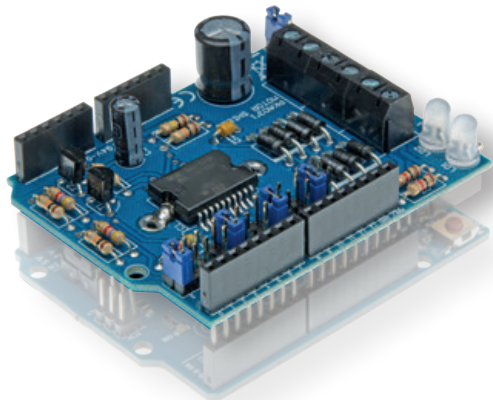


# KA03

ILLUSTRATED ASSEMBLY MANUAL HKA03IP1

## Motor & Power shield Arduino®



**Power shield that can drive: relays, solenoids, DC and stepper motors**

### Features

- For use with Arduino Due™, Arduino Uno™, Arduino Mega™
- Based on L298P dual full bridge driver IC
- Outputs: up to 2 DC motors or 1 bipolar stepper motor
- Power supply: external power or power from Arduino board

### Specifications

- Power supply: 7..46VDC
- Max current: 2A
- Dimensions: 68 x 53mm / 2.67 x 2.08"



**Search product**

Search Product

**Navigation**

- Home page
- Products
- Sales outlets
- Support
- Publications
- Jobs
- About us

News

**NEW INK3D LED COBE**

Cobekontrol software available for download [here!](#)

Posted on 04-06-12

[Read more...](#)

**velleman projects**

Velleman Projects  
All about the various open  
developments: kits, modules,  
instruments and home automation

Webal Kingdom -  
English (UK)

Change

**Velleman Projects Newsletter**

Are you an electronic enthusiast or simply interested in our kits, modules, modules and instruments?

Subscribe to our Newsletter and receive every month the latest news, new products & updates on Velleman Projects.

You will receive an email. Click on the link in that email to confirm your subscription.

Email:

Do you want to unsubscribe? Click on the 'unsubscribe' link in the footer of the last received newsletter from Velleman Projects.

velleman.eu

Supporter.eu

panel.eu

vellemanprojects.com

vellem.eu

forum.velleman.eu

**Advertisements**

WIN7 / WIN8  
Android Application



Subscribing our newsletter?, visit [www.vellemanprojects.eu](http://www.vellemanprojects.eu)



Participate our Velleman Projects Forum

**velleman projects**

**INSTRUMENTS**  
velleman projects kit

**Support Forum (ENFR)**

vellemanprojects.com

EN FR

Home | Register | Login

How many unread topics | View active topics

**Advanced** 93 topics and 970 posts

Author	Topic	Topics	Posts	Last post
Frank-Holter, Regenerato de Frank	Navigation 7 & 8 in an extension kit	1	1	Wed Dec 19, 2012 12:44 PM <a href="#">vellem.eu</a>
Frank-Holter	Vellem.eu On-line Home Automation	1	1	Fri Dec 14, 2012 12:07 PM <a href="#">vellem.eu</a>
<b>Vellem.eu Home Automation</b>	Control system for our new Vellem Home Automation System (Control)	404	2072	Tue Dec 11, 2012 12:00 PM <a href="#">vellem.eu</a>
<b>Kit Ordering projects - Products &amp; modules</b>				
General	For other topics, general topic and topics, new ideas	273	1328	Wed Dec 19, 2012 12:07 PM <a href="#">vellem.eu</a>
Audio Kit (Projects)	All audio related projects, amplifiers, radio modules	107	5405	Fri Dec 14, 2012 12:00 PM <a href="#">vellem.eu</a>
Kit Related Projects	The projects that are included in the KIT line interface kits	1428	6928	Fri Dec 14, 2012 12:00 PM <a href="#">vellem.eu</a>
Microcontroller Programmer - Expanding Projects	Microcontroller Programmer (PIC, AVR, ARM, etc.)	407	2104	Tue Dec 11, 2012 12:00 PM <a href="#">vellem.eu</a>
Remote applications	All about our remote control projects from regular remote to programmable links	281	1305	Fri Dec 14, 2012 12:00 PM <a href="#">vellem.eu</a>
Home Projects	Home automation projects, from light projects to remote control	624	3282	Fri Dec 14, 2012 12:00 PM <a href="#">vellem.eu</a>



**Velleman N.V.**  
**Legen Heirweg 33**  
**9890 Gavere**  
**(België)**

## assembly hints

### 1. Assembly (Skipping this can lead to troubles !)

Ok, so we have your attention. These hints will help you to make this project successful. Read them carefully.



#### 1.1 Make sure you have the right tools:

- A good quality soldering iron (25-40W) with a small tip.
- Wipe it often on a wet sponge or cloth, to keep it clean; then apply solder to the tip, to give it a wet look. This is called 'thinning' and will protect the tip, and enables you to make good connections. When solder rolls off the tip, it needs cleaning.
- Thin raisin-core solder. Do not use any flux or grease.
- A diagonal cutter to trim excess wires. To avoid injury when cutting excess leads, hold the lead so they cannot fly towards the eyes.
- Needle nose pliers, for bending leads, or to hold components in place.
- Small blade and Phillips screwdrivers. A basic range is fine.



For some projects, a basic multi-meter is required, or might be handy



#### 1.2 Assembly Hints :

- Make sure the skill level matches your experience, to avoid disappointments.
- Follow the instructions carefully. Read and understand the entire step before you perform each operation.
- Perform the assembly in the correct order as stated in this manual
- Position all parts on the PCB (Printed Circuit Board) as shown on the drawings.
- Values on the circuit diagram are subject to changes, the values in this assembly guide are correct\*
- Use the check-boxes to mark your progress.
- Please read the included information on safety and customer service

\* Typographical inaccuracies excluded. Always look for possible last minute manual updates, indicated as 'NOTE' on a separate leaflet.

#### 1.3 Soldering Hints :

1. Mount the component against the PCB surface and carefully solder the leads




2. Make sure the solder joints are cone-shaped and shiny



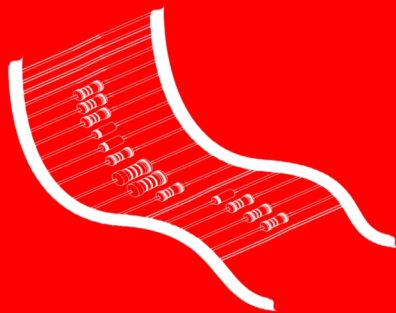3. Trim excess leads as close as possible to the solder joint





REMOVE THEM FROM THE TAPE ONE AT A TIME !

Included in this kit

**2. RESISTOR**


R1 : 120 (1 - 2 - 1 - B)

COLOUR	COLOUR NAME	1ST DIGIT/ STRIPE	2ND DIGIT/ STRIPE	3RD DIGIT/ STRIPE	MULTIPLIER STRIPE	TOLERANCE 4TH
Black	BLACK	0	0	0	x1	1%
Brown	BROWN	1	1	1	x10	
Red	RED	2	2	2	x100	
Orange	ORANGE	3	3	3	x1.000	
Yellow	YELLOW	4	4	4	x10.000	
Green	GREEN	5	5	5	x100.000	
Blue	BLUE	6	6	6	x1.000.000	

**DO NOT BLINDLY FOLLOW THE ORDER OF THE COMPONENTS ONTO THE TAPE. ALWAYS CHECK THEIR VALUE ON THE PARTS LIST!**


## 1 CONSTRUCTION

### 1 Resistors

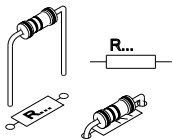

- R1: 4K7 (4 - 7 - 2 - B)
- R2: 10K (1 - 0 - 3 - B)
- R3: 4K7 (4 - 7 - 2 - B)
- R4: 4K7 (4 - 7 - 2 - B)
- R5: 10K (1 - 0 - 3 - B)
- R6: 4K7 (4 - 7 - 2 - B)
- R7: 1K (1 - 0 - 2 - B)
- R8: 1K (1 - 0 - 2 - B)
- R9: 100K (1 - 0 - 4 - B)
- R10: 10K (1 - 0 - 3 - B)

### 2 Ceramic capacitors

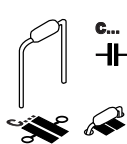

- C1: 100nF (104)

### 3 Shottky diode




- D1: 1N5819
- D2: 1N5819
- D3: 1N5819
- D4: 1N5819
- D5: 1N5819
- D6: 1N5819
- D7: 1N5819
- D8: 1N5819

### 4 Transistors



- T1: BC547B
- T2: BC547B

### 5 Male header

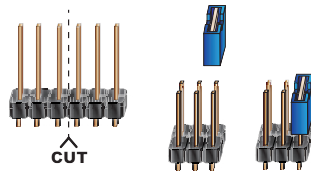

- SK8... SK10: 2x3pin





- 3pin




INTERNAL  
power from Arduino  
Max. 2A




## 6 Female header

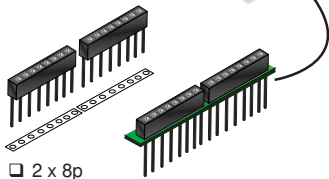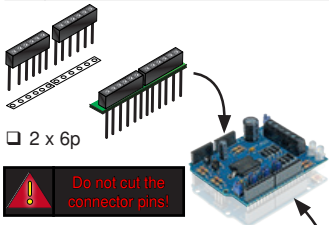


## 7 LED's

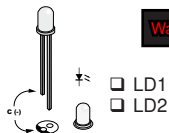



## 8 Terminal blocks

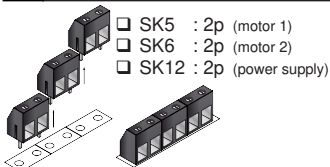


## 10 Dual Full Bridge driver

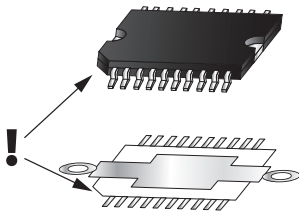


□ IC1: L298P

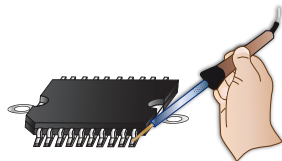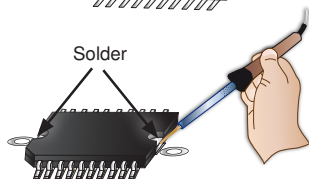

## 9 Electrolytic capacitors

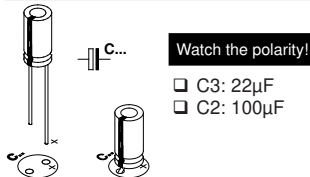



## II CONNECTION DIAGRAM

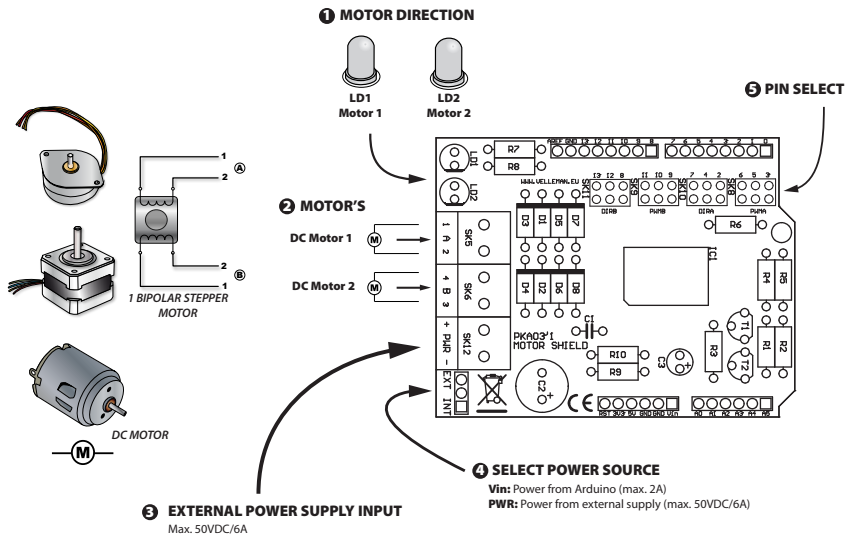

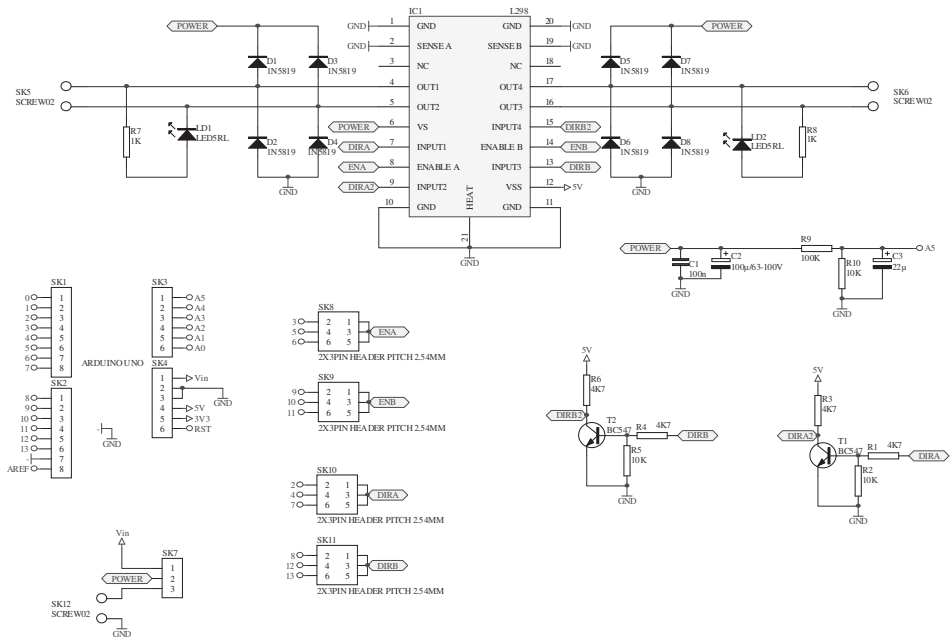
DOWNLOAD SAMPLE CODE FROM KA03 PAGE ON [WWW.VELLEMAN.BE](http://WWW.VELLEMAN.BE)






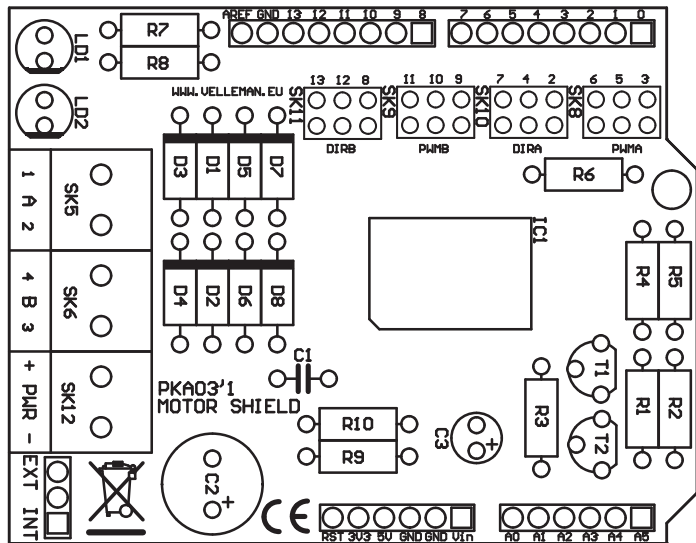


# Leds and how to use them

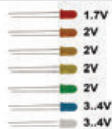

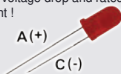Leds feature a specific voltage drop, depending on type and colour. Check the datasheet for exact voltage drop and rated current !



Never connect leds in parallel

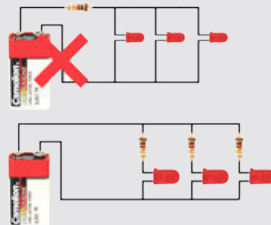

## How to Calculate the series resistor:

Example: operate a red led (1.7V) on a 9Vdc source.

Required led current for full brightness: 5mA (this can be found in the datasheet of the led)

$$\frac{\text{Supply voltage (V) - led voltage (V)}}{\text{required current (A)}} = \text{series resistance (ohms)}$$

$$\rightarrow \frac{9V - 1.7V}{0.005A} = 1460 \text{ ohm}$$

closest value :  
use a 1k5 resistor

Required resistor power handling=  
voltage over resistor x current passed trough resistor


$$\rightarrow (9V - 1.7V) \times 0.005A = 0.036W$$

a standard 1/4W resistor  
will do the job

## LEDs in series:

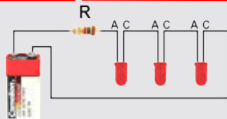Example: 3 x red led (1.7V) on 9V battery

Required led current for full brightness: 5mA  
(this can be found in the datasheet of the led)




$$\frac{\text{Supply voltage (V) - (number of leds x led voltage (V))}}{\text{required current (A)}} = \text{series resistance (ohms)}$$

$$\rightarrow \frac{9V - (3 \times 1.7V)}{0.005A} = 780 \text{ ohm}$$


use an  
820 ohm resistor
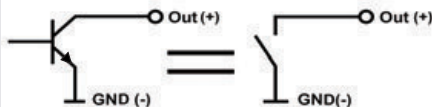
## open collector outputs

An open collector output can be compared to a switch which switches to ground when operated



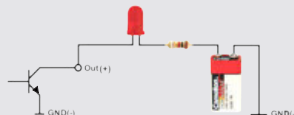Example: How to switch an LED by means of an open collector output





The new Velleman Projects catalogue is  
now available. Download your copy here:  
[www.vellemanprojects.eu](http://www.vellemanprojects.eu)



Modifications and typographical errors reserved - © Velleman nv. HKA03'IP (Rev.1)  
Velleman NV, Legen Heirweg 33 - 9890 Gavere.